

Noise 4

Exercises

TI Precision Labs – Op Amps



1. Is current noise or voltage noise dominant for the circuit below?
2. Is 1/f or broadband dominant?
3. Is resistor or op amp voltage noise dominant?
4. Calculate the total noise using appropriate simplifications.

ELECTRICAL CHARACTERISTICS: $V_S = \pm 2.25\text{ V}$ to $\pm 4\text{ V}$ ($V_S = +4.5\text{ V}$ to $+8\text{ V}$)

At $T_A = +25^\circ\text{C}$, $V_{CM} = V_{OUT} = V_S / 2$, and $R_{LOAD} = 10\text{ k}\Omega$ connected to $V_S / 2$, unless otherwise noted.

PARAMETER	TEST CONDITIONS	OPA192			UNIT
		MIN	TYP	MAX	
NOISE					
E_n Input voltage noise	$(V-) - 0.1\text{ V} < V_{CM} < (V+) - 3\text{ V}$, $f = 0.1\text{ Hz to } 10\text{ Hz}$		1.30		μV_{PP}
	$(V+) - 1.5\text{ V} < V_{CM} < (V+) + 0.1\text{ V}$, $f = 0.1\text{ Hz to } 10\text{ Hz}$		4		μV_{PP}
e_n Input voltage noise density	$(V-) - 0.1\text{ V} < V_{CM} < (V+) - 3\text{ V}$	$f = 100\text{ Hz}$		10.5	$\text{nV}/\sqrt{\text{Hz}}$
		$f = 1\text{ kHz}$		5.5	$\text{nV}/\sqrt{\text{Hz}}$
	$(V+) - 1.5\text{ V} < V_{CM} < (V+) + 0.1\text{ V}$	$f = 100\text{ Hz}$		32	$\text{nV}/\sqrt{\text{Hz}}$
		$f = 1\text{ kHz}$		12.5	$\text{nV}/\sqrt{\text{Hz}}$
i_n Input current noise density	$f = 1\text{ kHz}$		1.5		$\text{fA}/\sqrt{\text{Hz}}$
FREQUENCY RESPONSE					
GBW Unity gain bandwidth			10		MHz

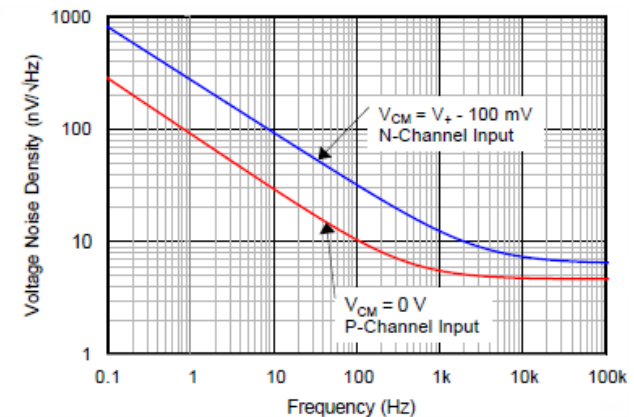
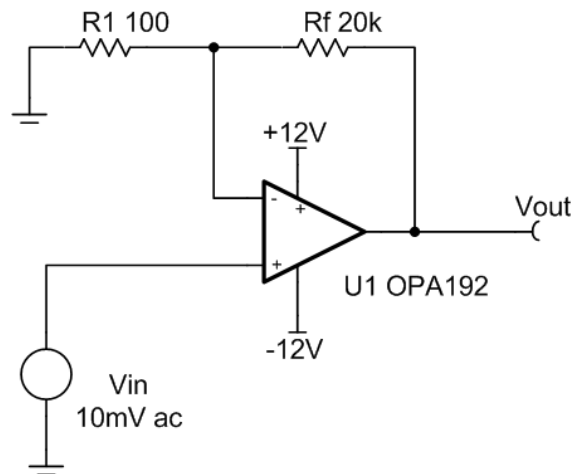


Figure 17. INPUT VOLTAGE NOISE SPECTRAL DENSITY vs FREQUENCY



5. Is current noise or voltage noise dominant for the circuit below?
6. Is 1/f or broadband dominant?
7. Is resistor or op amp voltage noise dominant?
8. Calculate the total rms noise at the output.

ELECTRICAL CHARACTERISTICS: $V_S = \pm 2.25V$ to $\pm 18V$

BOLDFACE limits apply over the specified temperature range, $T_A = -40^\circ C$ to $+125^\circ C$.

At $T_A = +25^\circ C$, $R_L = 10k\Omega$ connected to midsupply, $V_{CM} = V_{OUT} =$ midsupply, unless otherwise noted.

PARAMETER	CONDITIONS	Standard Grade OPA211AI, OPA2211AI			High Grade OPA211I(1)			UNIT
		MIN	TYP	MAX	MIN	TYP	MAX	
NOISE								
Input Voltage Noise	e_n		80		80			nV _{pp}
Input Voltage Noise Density	$f = 0.1Hz$ to $10Hz$		2		2			nV/ \sqrt{Hz}
	$f = 100Hz$		1.4		1.4			nV/ \sqrt{Hz}
	$f = 1kHz$		1.1		1.1			nV/ \sqrt{Hz}
Input Current Noise Density	i_n		3.2		3.2			pA/ \sqrt{Hz}
	$f = 10Hz$		1.7		1.7			pA/ \sqrt{Hz}
	$f = 1kHz$							
FREQUENCY RESPONSE								
Gain-Bandwidth Product	GBW	$G = 100$	80		80			MHz
		$G = 1$	45		45			MHz

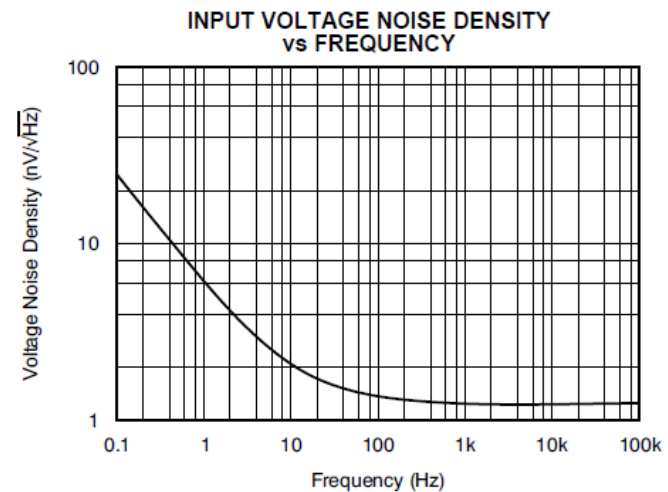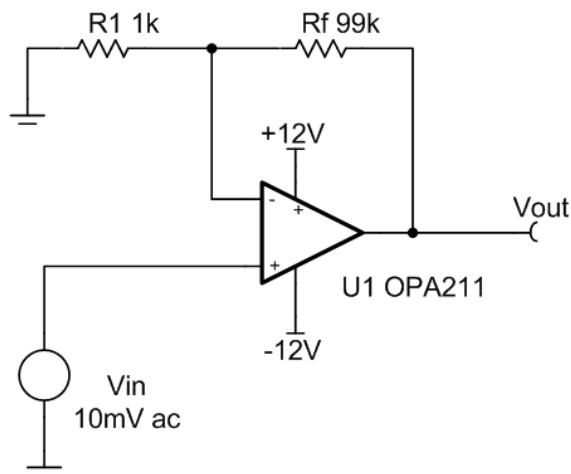

9. Is the input or output stage dominant?
10. Is current noise or voltage noise dominant for the circuit below?
11. Is 1/f or broadband dominant?
12. Is resistor or op amp voltage noise dominant?
13. Calculate the total noise using appropriate simplifications.

ELECTRICAL CHARACTERISTICS:

High-Voltage Operation, $V_S = \pm 4\text{ V to } \pm 18\text{ V}$ ($V_S = +8\text{ V to } +36\text{ V}$)

At $T_A = +25^\circ\text{C}$, $R_L = 10\text{ k}\Omega$ connected to $V_S / 2^{(1)}$, and $V_{CM} = V_{OUT} = V_S / 2^{(1)}$, unless otherwise noted.

PARAMETER	CONDITIONS	MIN	TYP	MAX	UNIT
NOISE					
e_n	Input voltage noise	f = 0.1 Hz to 10 Hz		250	nV _{pp}
		f = 0.1 Hz to 10 Hz		40	nV _{rms}
	Input voltage noise density	f = 1 kHz		8.8	nV/ $\sqrt{\text{Hz}}$
i_n	Input current noise density	f = 1 kHz		7	fA/ $\sqrt{\text{Hz}}$
FREQUENCY RESPONSE					
GBW	Gain-bandwidth product			2	MHz


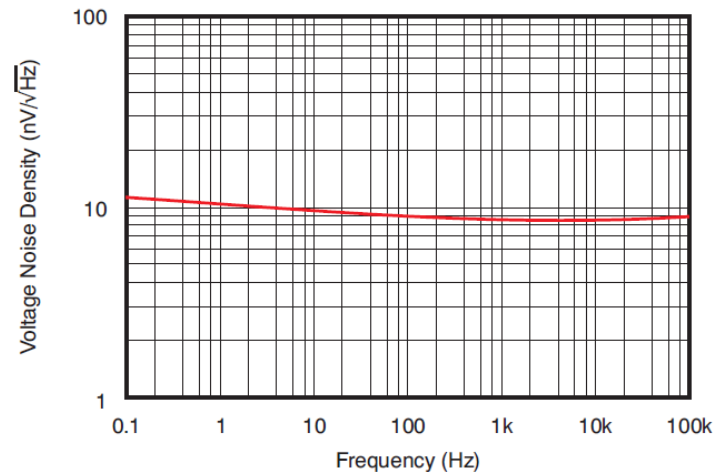


Figure 18. INPUT VOLTAGE NOISE SPECTRAL DENSITY vs FREQUENCY

Noise 4

Solutions

TI Precision Labs – Op Amps

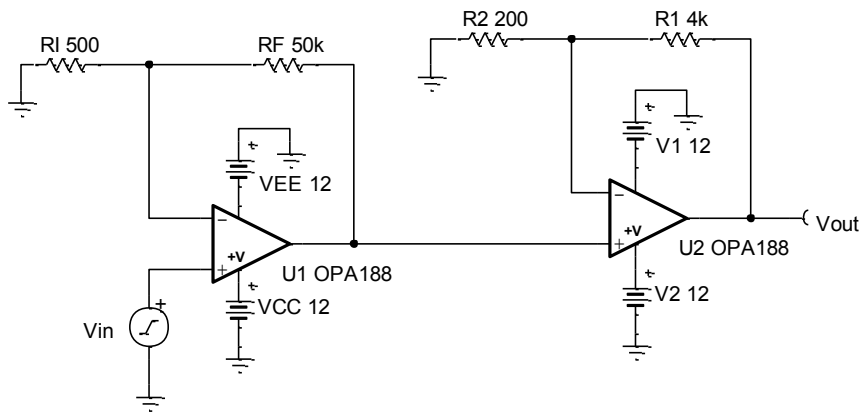

1. Is current noise or voltage noise dominant for the circuit below?

$$R_{eq} = R_f || R_1 \approx 100\Omega$$

$$e_{ni} = R_{eq} \cdot i_n = (100\Omega)(1.5 \text{ fA}/\sqrt{\text{Hz}}) = 300 \text{ fV}/\sqrt{\text{Hz}} \text{ or } 0.00015 \text{ nV}/\sqrt{\text{Hz}}$$

$$5.5 \text{ nV}/\sqrt{\text{Hz}} \gg 0.00015 \text{ nV}/\sqrt{\text{Hz}} \quad \Leftrightarrow \quad e_{nv} \gg e_{ni}$$

Thus voltage noise is dominant

2. Is 1/f or broadband dominant?

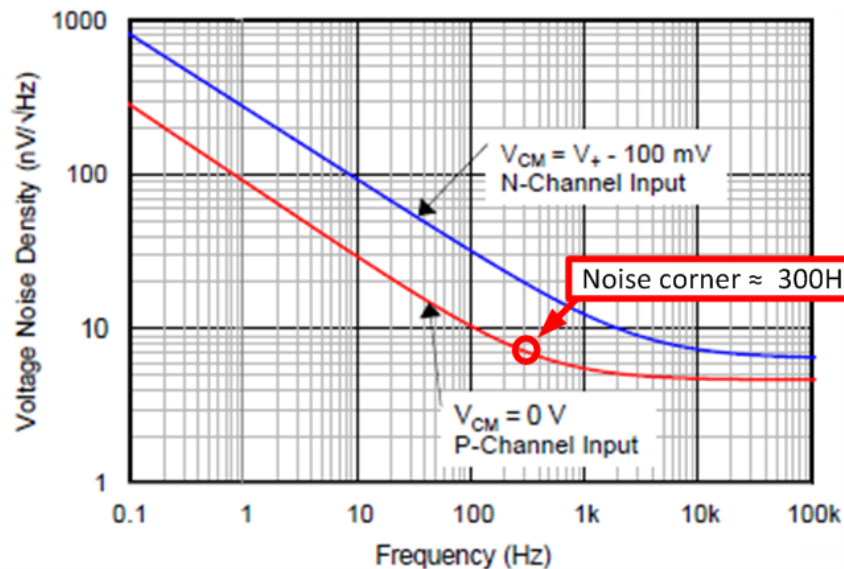


Figure 17. INPUT VOLTAGE NOISE SPECTRAL DENSITY vs FREQUENCY

$$G_n = \frac{R_f}{R_1} + 1 = \frac{20\text{k}\Omega}{100\Omega} + 1 = 201$$

$$f_c = \frac{\text{GBW}}{G_n} = \frac{10\text{MHz}}{201} = 49.8\text{kHz}$$

$$\text{BW}_n = K_n \cdot f_c = (1.57)(49.8\text{kHz}) = 78.2\text{kHz}$$

$$78.2\text{kHz} \gg 300\text{Hz} \quad \Leftrightarrow \quad \text{BW}_n \gg f_f$$

Thus broadband noise is dominant

3. Is resistor or op amp voltage noise dominant?


Refer to the data sheet table. Notice that the op amp voltage noise is dependent on common mode voltage. $V_{cm} = 0V$ in this example, so noise is $5.5nV/\sqrt{rtHz}$. The equivalent feedback resistance is approximately 100Ω , so using the chart below the resistor noise is $2nV/\sqrt{rtHz}$.

$1.3nV/\sqrt{rtHz} \times 3 = 3.9nV/\sqrt{rtHz}$

(apply Rule 1)

$5.5nV/\sqrt{rtHz} \gg 1.3nV/\sqrt{rtHz}$

(op amp voltage noise is dominant)

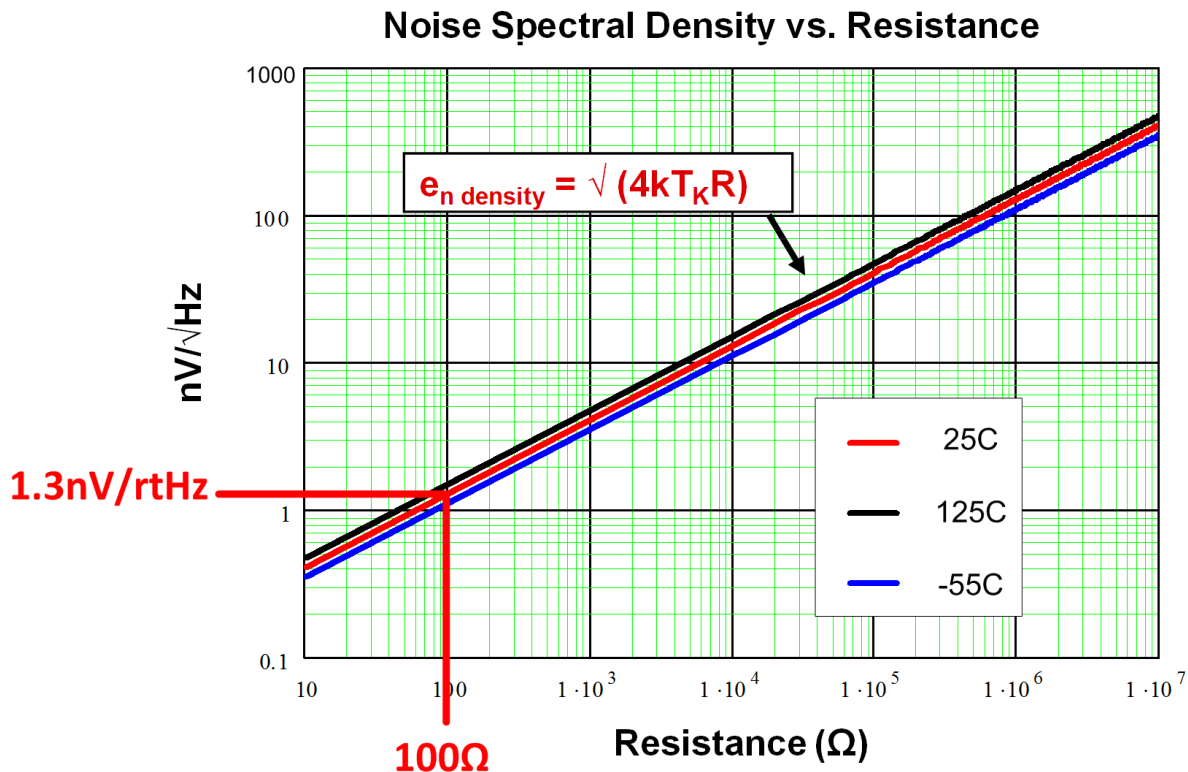

4. Calculate the total noise using appropriate simplifications.

$$G_n = \frac{R_f}{R_1} + 1 = \frac{20\text{k}\Omega}{100\Omega} + 1 = 201$$

$$f_c = \frac{\text{GBW}}{G_n} = \frac{10\text{MHz}}{201} = 49.8\text{kHz}$$

$$\text{BW}_n = K_n \cdot f_c = (1.57)(49.8\text{kHz}) = 78.2\text{kHz}$$

$$E_n = (G_n)(e_n)\sqrt{\text{BW}_n} = (201)(5.5 \text{ nV}/\sqrt{\text{Hz}})\sqrt{(78.2\text{kHz})} = 309\mu\text{V rms}$$

$$E_{npp} = 6E_n = 6(309\mu\text{V rms}) = 1.85\text{mVpp}$$

5. Is current noise or voltage noise dominant for the circuit below?


$$R_{eq} = R_f || R_1 \approx 1k\Omega$$

$$e_{ni} = R_{eq} \cdot i_n = (1k\Omega)(1.7 \text{ pA}/\sqrt{\text{Hz}}) = 1.7 \text{ nV}/\sqrt{\text{Hz}}$$

$$e_{nv} = 1.1 \text{ nV}/\sqrt{\text{Hz}} \text{ and } e_{ni} = 1.7 \text{ nV}/\sqrt{\text{Hz}} \Rightarrow e_{nv} \not\gg e_{ni}$$

$e_{nv} \approx e_{ni} \Rightarrow$ Thus both voltage noise and current noise need to be considered

6. Is 1/f or broadband dominant?

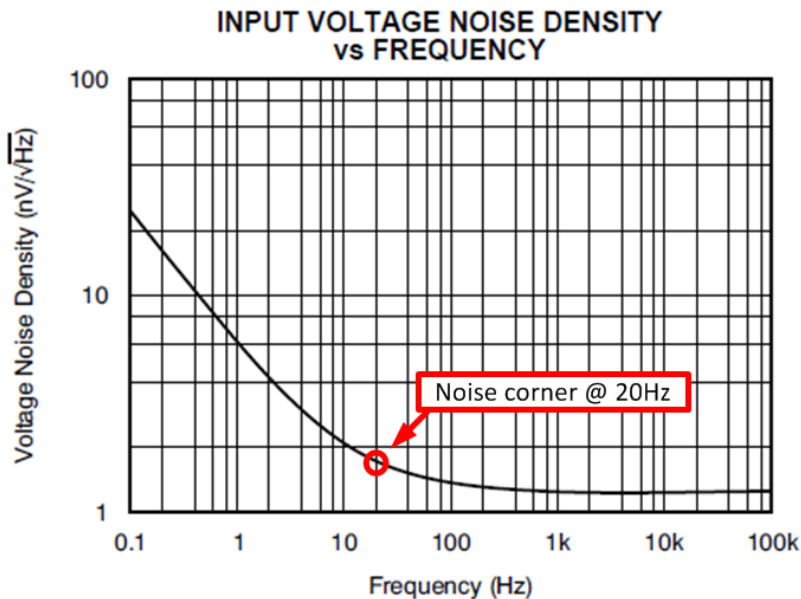

$$G_n = \frac{R_f}{R_1} + 1 = \frac{99k\Omega}{1k\Omega} + 1 = 101$$

$$f_c = \frac{GBW}{G_n} = \frac{80\text{MHz}}{101} = 792\text{kHz}$$

$$BW_n = K_n \cdot f_c = (1.57)(792\text{kHz} *) = 1.24\text{MHz}$$

$$1.24\text{MHz} \gg 20\text{Hz} \Rightarrow BW_n \gg f_f$$

Thus broadband noise is dominant

7. Is resistor or op amp voltage noise dominant?

$$e_n = 1.1\text{nV}/\sqrt{\text{rtHz}} \quad (\text{op amp noise})$$


$$e_{nr} = 4\text{nV}/\sqrt{\text{rtHz}} \quad (\text{resistor noise})$$

$$4\text{nV}/\sqrt{\text{rtHz}} \times 3 = 12\text{nV}/\sqrt{\text{rtHz}} \quad (\text{apply Rule 1})$$

The op amp noise needs to be greater than $12\text{nV}/\sqrt{\text{rtHz}}$ to be dominant.

In this case, resistor noise dominates $e_{nr} \gg e_n$

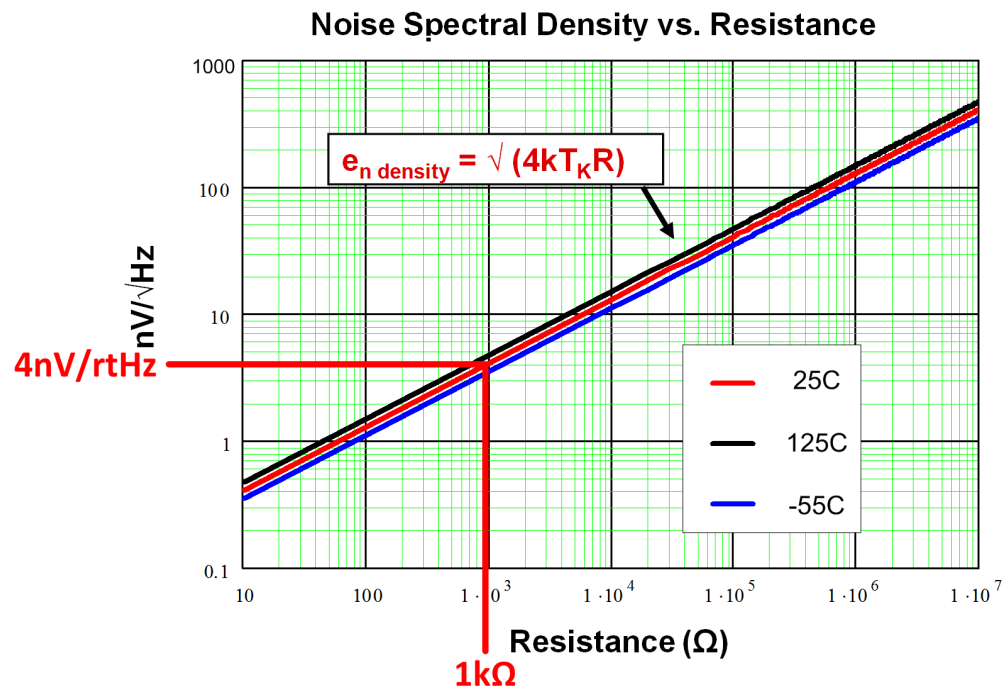Normally, it is recommended to reduce the feedback impedance to ensure that the op amp noise dominates. The only concern is that lower feedback impedances translate to larger output current requirements.



8. Calculate the total rms noise at the output.

$$e_{ni} = 1.7 \text{ nV}/\sqrt{\text{Hz}}$$

$$e_{nr} = 4 \text{ nV}/\sqrt{\text{Hz}}$$

$$e_{nv} = 1.1 \text{ nV}/\sqrt{\text{Hz}}$$

$$e_{n_tot} = \sqrt{e_{ni}^2 + e_{nr}^2 + e_{nv}^2} = \sqrt{(1.7)^2 + (4)^2 + (1.1)^2} = 4.5 \text{ nV}/\sqrt{\text{Hz}}$$

$$E_{n_tot} = (G_n)(e_{n_tot})\sqrt{BW_n} = (100) \left(\frac{4.5 \text{ nV}}{\sqrt{\text{Hz}}} \right) \sqrt{1.24 \text{ MHz}} = 501 \mu\text{V rms}$$

9. Is the input or output stage dominant?

The input stage and the output stage both use the same amplifier. This makes the comparison easy. If a higher noise amplifier were used in the output stage more calculations may be required. In this case, just look at the first stage gain. If it is greater than 3 than the input stage will be dominant (Rule 1). In this case the noise gain of the input stage is 101, so the input stage is dominant. In subsequent calculation we will only consider the input stage. The gain of the output stage only need be considered to calculation the output noise. The noise sources in the second stage are ignored.

Note: In some cases the noise from the second stage may play a role if the bandwidth of the second stage is significantly wider than the first stage. In this case a Cf filter may be advisable.

10. Is current noise or voltage noise dominant for the circuit below?

$$R_{eq} = R_f || R_1 \approx 500\Omega$$

$$e_{ni} = R_{eq} \cdot i_n = (500\Omega)(7 \text{ fA}/\sqrt{\text{Hz}}) = 0.0035 \text{ nV}/\sqrt{\text{Hz}}$$

$$e_{nv} = 8.8 \text{ nV}/\sqrt{\text{Hz}} \text{ and } e_{ni} = 0.0035 \text{ nV}/\sqrt{\text{Hz}} \Rightarrow e_{nv} \gg e_{ni}$$

Op amp voltage noise is dominant

11. Is 1/f or broadband dominant?

This is a trick question. The OPA188 is a zero drift amplifier and does not have 1/f noise. Notice that the spectral density curve is relatively flat down to 0.1Hz. So in this case broadband is definitely dominant because there is no 1/f noise.

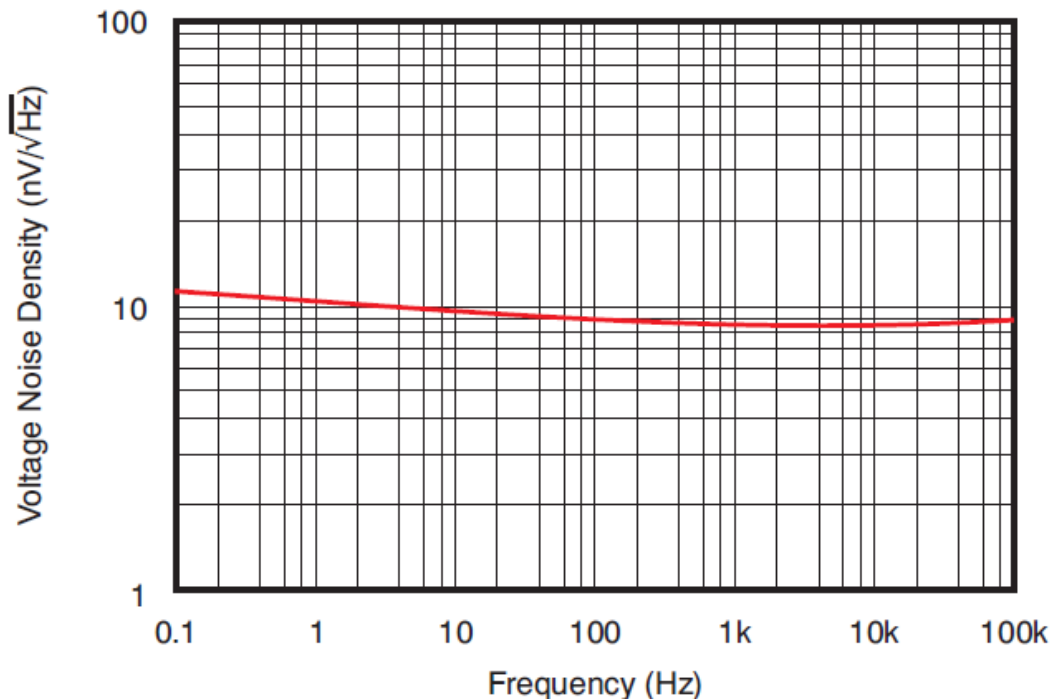


Figure 18. INPUT VOLTAGE NOISE SPECTRAL DENSITY vs FREQUENCY


12. Is resistor or op amp voltage noise dominant?

Op amp noise is 8.8nV/rtHz. The equivalent feedback resistance is approximately 500Ω, so using the chart below the resistor noise is 3nV/rtHz.

3nV/rtHz x 3 = 9nV/rtHz (apply Rule 1)

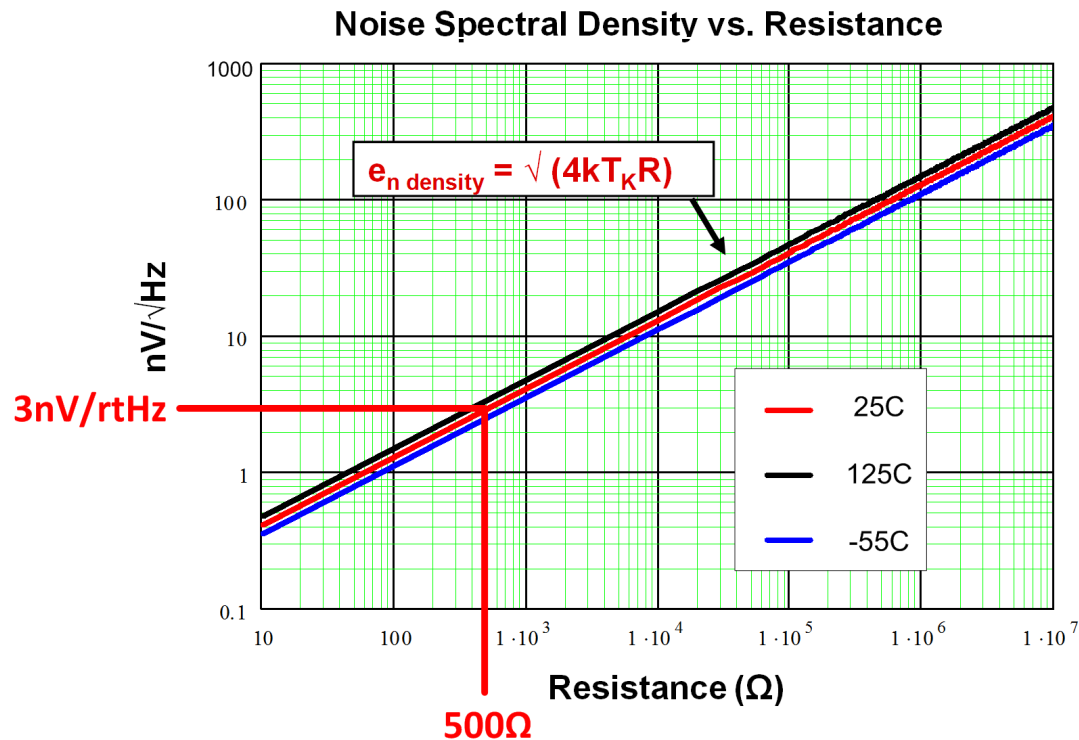8.8nV/rtHz >> 3nV/rtHz (Op amp noise almost dominant)

Technically the op amp noise is not quite 3x the resistor noise. However, it's close so let's assume that it's dominant. In a real world design you might further reduce the feedback. However, you don't need to reduce much.



13. Calculate the total noise using appropriate simplifications.

$$G_{n1} = \frac{R_f}{R_1} + 1 = \frac{50\text{k}\Omega}{500\Omega} + 1 = 101$$

$$G_{n2} = \frac{R_f}{R_1} + 1 = \frac{4\text{k}\Omega}{200\Omega} + 1 = 21$$

$$f_{c1} = \frac{\text{GBW}}{G_n} = \frac{2\text{MHz}}{101} = 19.8\text{kHz}$$

$$\text{BW}_n = K_n \cdot f_c = (1.57)(19.8\text{kHz}) = 31.1\text{kHz}$$

$$E_n = (G_{n1})(G_{n2})(e_n)\sqrt{\text{BW}_n} = (101)(21)(8.8 \text{ nV}/\sqrt{\text{Hz}})\sqrt{(15.6\text{kHz})} = 3.30\text{mV rms}$$

$$E_{npp} = 6E_n = 6(4.64\text{m} * \text{V rms}) = 27.8\text{mVpp}$$